

Series Resistance Compensation

The series resistance (R_s) of the patch pipette produces two undesired effects in whole-cell voltage clamp recordings:

(i) R_s introduces a voltage error, causing the cell membrane voltage (V_m) to deviate from the desired clamping voltage whenever ionic current flows. This voltage error is often called an “IR” drop since it is given by Ohms law ($V=IR$), where I is the patch pipette current;

(ii) R_s lowers the temporal resolution of the voltage clamp, often to the extent that rapid physiologic processes cannot be accurately measured. The temporal resolution is quantified by the access time constant $\tau_a = R_s \cdot C_m$, where C_m is the cell capacitance. (Note that increasing τ_a , either by increasing R_s and/or C_m , decreases the temporal resolution).

These two effects are collectively referred to here as “ R_s errors”.

The goal of R_s compensation

The goal of R_s compensation is to reduce, and ideally eliminate, R_s errors from whole-cell voltage clamp recordings. Therefore, R_s compensation should reduce (and ideally eliminate) the R_s voltage error when ionic current flows, and it should increase the temporal resolutions of the voltage clamp by reducing τ_a .

Standard R_s compensation – the usual approach

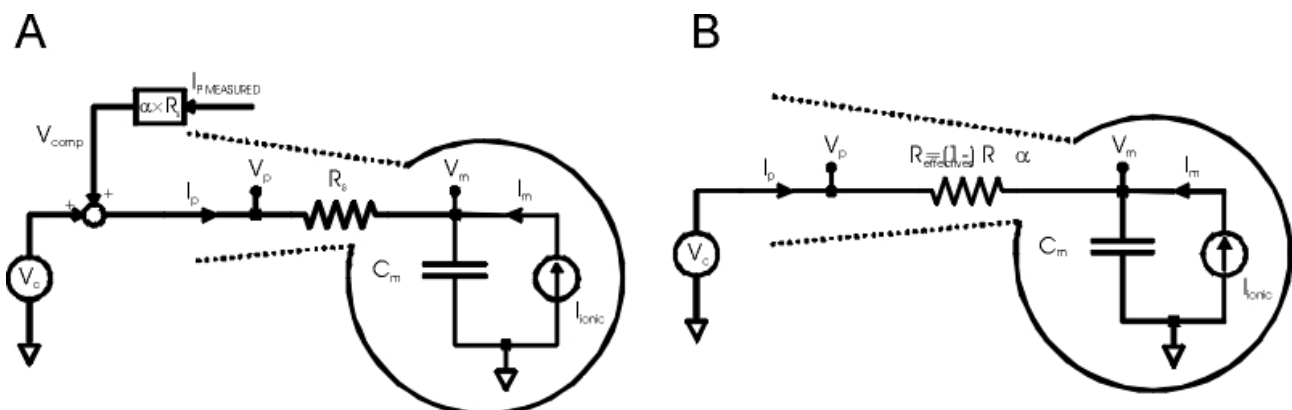


Fig 1 Standard R_s compensation

A. Voltage clamp of pipette and cell, with standard R_s compensation added as positive feedback. B. Equivalent circuit.

V_c = command voltage; I_p = pipette current; V_p = pipette voltage; R_s = pipette series resistance; V_m = cell membrane voltage; C_m = cell capacitance; I_m = cell membrane ionic current; $I_{p,measured}$ = measured pipette current; α = R_s compensation scaling factor [0,1]; $R_{effective}$ = effective series resistance.

Standard R_s compensation (Fig 1A) is the usual approach commercial patch clamps employ to address R_s errors. Referring to Fig 1A, a fraction of the pipette “IR” drop is continuously computed ($I_{p,measured} \cdot R_s \cdot \alpha$) and is then added to the voltage clamp command as a correction signal, forming a positive feedback loop. The result of standard R_s compensation is summarized in the equivalent circuit of Fig 1B, which shows that the positive feedback loop acts to reduce the effective value of R_s by the factor $(1-\alpha)$. For example, if α is set to 0.8 (80% R_s compensation), $R_{effective} = (1-0.8) \cdot R_s = 0.2 \cdot R_s$ (20%

of the original value R_s). Therefore, 80% R_s compensation reduces R_s voltage errors by 80% and simultaneously increases the temporal resolution by the same amount ($\tau_{\text{effective}} = R_{\text{effective}} \cdot C_m$).

Standard R_s compensation hits the “speed wall”

Fig 1B predicts that Standard R_s compensation should completely eliminate R_s errors when α is set to 1 (i.e. the full IR drop across the electrode is used as positive feedback) since the effective R_s is then predicted to be equal to 0. In practice standard R_s compensation can't do this because the entire positive feedback loop becomes unstable when α is increased beyond ~ 0.9 (90% R_s compensation).

This effect is shown graphically in Fig 2, which plots membrane voltage in response to ionic current steps with increasing amounts of R_s compensation.

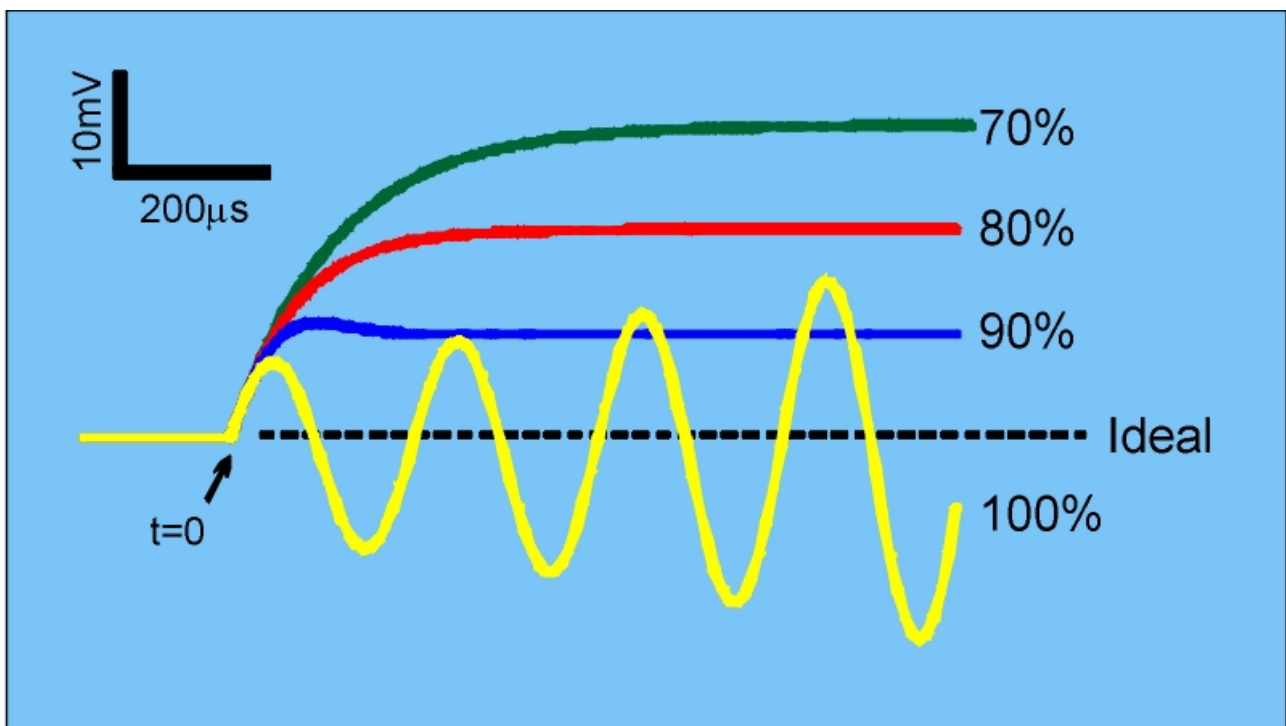


Fig 2 Voltage error with Standard R_s compensation

R_s voltage error ($V_m - V_{\text{hold}}$) in response to repetitive 10nA ionic current steps (applied at $t=0$) with increasing amounts of standard R_s compensation.

Circuit as in Fig 1A. Ionic = 10nA step applied at $t=0$; $R_s = 10\text{Meg}$; $C_m = 50\text{pF}$; $V_{\text{hold}} = \text{constant}$; bandwidth of $I_{\text{pmeasured}} = 50\text{kHz}$;

As R_s compensation is increased, the R_s voltage error is reduced and the voltage clamp speed is increased, but beyond 90% R_s compensation the circuit produces unbounded oscillations which would kill the cell (yellow trace). Because of this, it is impossible for standard R_s compensation to fully eliminate the IR drop across the patch pipette.

A clue as to why this occurs is to note that standard R_s compensation tries to reduce the effective access time constant ($\tau_{\text{effective}}$) to 0 as R_s compensation approaches 100%. This is equivalent to creating a voltage clamp that responds instantaneously. Instantaneous response (or infinite bandwidth) is of course not possible for any physical system. A full numerical analysis (see, for example, the appendix in Sherman, et al) shows

that stable R_s compensation requires the bandwidth of $I_{p\text{measured}}$ (used to create the feedback signal) to be at least five times the compensated voltage clamp bandwidth. Since the bandwidth of $I_{p\text{measured}}$ is limited by the electronics, the voltage clamp speed attainable with standard R_s compensation is limited as well, as is the maximum percentage R_s compensation. Therefore, standard R_s compensation always leaves a residual, finite R_s voltage error in whenever ionic current flows.

The Alembic R_s compensator™ eliminates the “speed wall”

The great utility of the R_s compensator is that it eliminates the “speed wall” described above which limits standard R_s compensation. Fig 3 illustrates improvement:

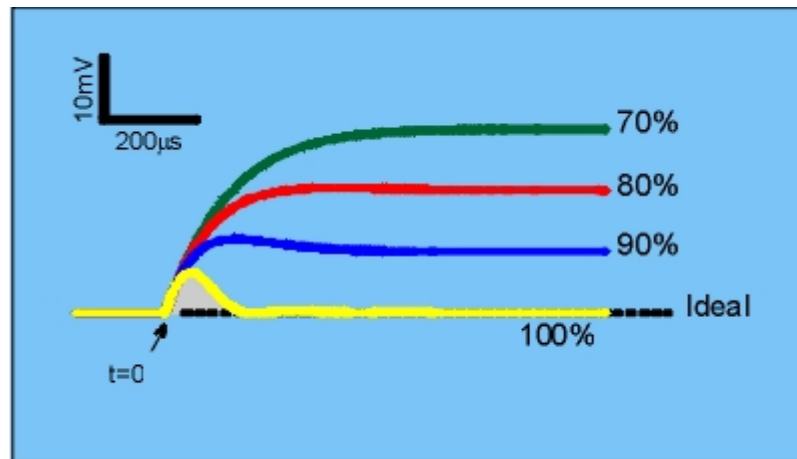


Fig 3 Voltage error with the R_s Compensator

R_s voltage error using the R_s compensator. All other parameters as described in Fig 2.

Comparing Figs 2 and 3 reveal similar performance below 90% R_s compensation. However, the R_s compensator allows 100% R_s compensation to be achieved whereas standard R_s compensation oscillates. At 100% R_s compensation (yellow trace, Fig 3), there is a transient R_s voltage error for $\sim 200\mu\text{s}$ (grayed “error zone”) after which the R_s voltage is error eliminated, as shown by the trace returning to the ideal “baseline” level. Significantly, the R_s compensator eliminates voltage error regardless of the magnitude of the ionic current flowing through the patch pipette.

What’s going on?

Standard R_s compensation oscillates because the voltage clamp bandwidth increases without limit as R_s compensation approaches 100%. In contrast, the R_s compensator limits the voltage clamp bandwidth at 100% R_s compensation, thereby avoiding the stability constraint (See the Theory section of US patent 4,700,427 for a mathematical derivation of the R_s compensator). In practice, the R_s compensator allows the voltage clamp bandwidth to be selected, such that higher bandwidths result in faster elimination of the R_s voltage error (i.e. the amplitude and duration of the gray “error zone” in Fig 3 is reduced). Going to the extreme of trying to eliminate the “error zone” altogether brings about the same instability associated with standard R_s compensation. In other words, in the limit of very high voltage clamp bandwidths, standard R_s compensation and the R_s compensator are equivalent.

Rs compensator Benefits

Ease of Use

The wide stability of the Rs compensator makes it very easy to use and tune in comparison to standard Rs compensation. Even at full Rs compensation, the Rs compensator remains stable as pipette conditions shift during an experiment (fluid level, whole-cell access resistance, etc). In contrast, small changes in pipette capacitance or series resistance very quickly cause standard Rs compensation to oscillate and kill the cell.

Voltage clamp control large, fast currents

The Rs compensator makes it much easier to voltage clamp large, regenerative currents, such as I_{Na} , under physiologic conditions. When clamping regenerative currents such as I_{Na} , Rs voltage errors of only 1-2 mV will trigger a cellular action potential with complete loss of the voltage clamp. Since standard Rs compensation, even pushed to its limit, nearly always leaves a voltage error greater than this threshold, other means must be used to further reduce this voltage error so as to maintain voltage control. Routine methods employed, such as lowering Na^+ gradients or cooling the entire preparation, introduce non-physiologic conditions that can compromise the validity of the experiment. Even then, it is still extremely difficult to maintain voltage control in excitable cells. In contrast, the Rs CompensatorTM eliminates Rs errors in $< 200\mu s$, independent of the magnitude of the ionic current. It is therefore possible to voltage clamp very large Na^+ current under physiologic temperatures concentration gradients while maintaining voltage control.